Translations:Pet that lights up upon interaction/34/en

Connect the negative leg of the LED to GND on the board, using a male/female jumper wire